ECE 413: Intro to VLSI

Assignment 1: Transistor Layout Introduction

Roderick Renwick



October 03, 2019 Fall 2019

Honor Code:		
I have neither	given nor received unauthorized assistance on this graded report.	
\mathbf{v}	Dodowialz Donyvialz	

Table of Contents

Table of Contents	2
NMOS	3
PMOS	4
CMOS Inverter	5
Cascaded CMOS Inverters	7
DRC Files	8
Conclusion	9

NMOS

The following figure shows an NMOS transistor layout.

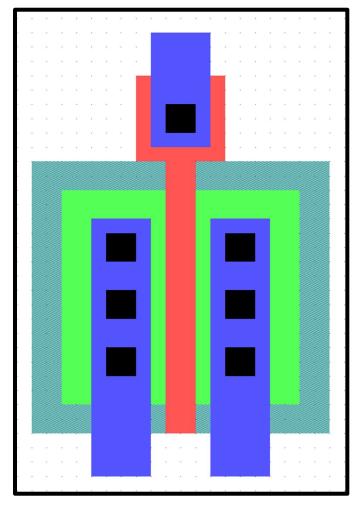


Figure-1: NMOS

Here are the resulting cross section views for the NMOS transistor shown above.

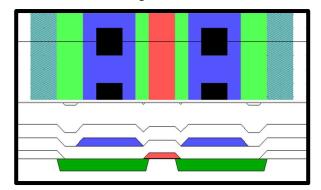


Figure-2: Horizontal Cross-Section of NMOS

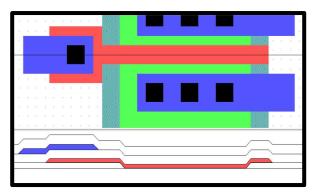


Figure-3: Vertical Cross-Section of NMOS

PMOS

The following figure shows a PMOS transistor layout (noting the N-Well layer on top of the substrate).

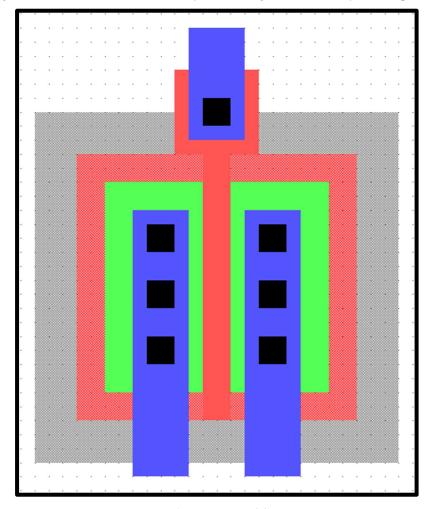


Figure-4: PMOS

Here are the resulting cross section views for the PMOS transistor shown above.

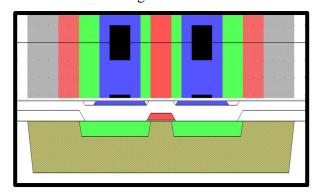


Figure-5: Horizontal Cross-Section of PMOS

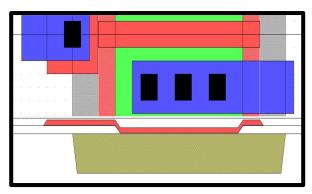


Figure-6: Vertical Cross-Section of PMOS

CMOS Inverter

The following figure shows a CMOS Inverter transistor layout made from the NMOS and PMOS. Note that the PMOS transistor is always connected to power, while the NMOS transistor is always grounded.

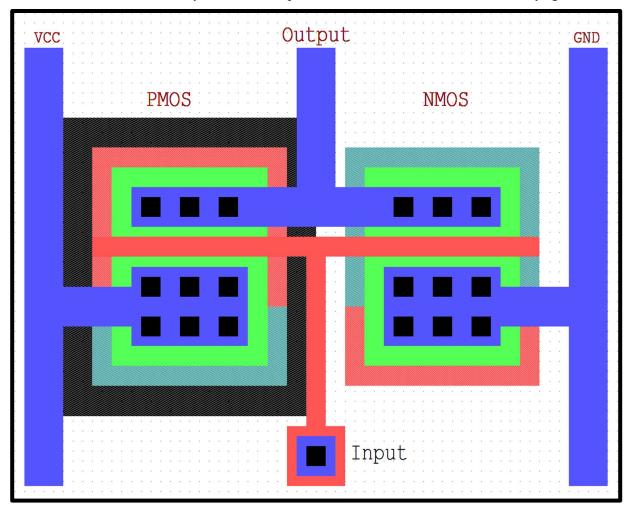


Figure-7: CMOS Inverter

Here are the resulting cross section views for the CMOS Inverter transistor shown on the previous page.

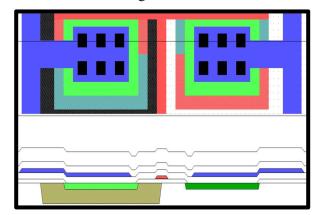


Figure-8: Horizontal Cross-Section of CMOS

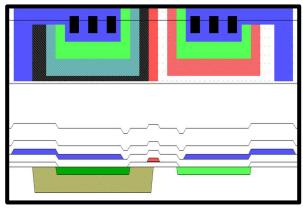


Figure-9: Horizontal Cross-Section of CMOS

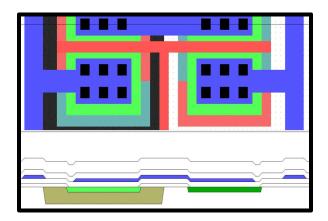


Figure-10: Metal1 Cross-Section of CMOS

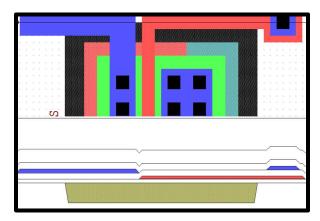


Figure-11: I/O Cross-Section of CMOS

Cascaded CMOS Inverters

The following figure shows three cascaded CMOS Inverter transistors. Note that the outputs of the prior CMOS drive the inputs of the following CMOS from left to right.

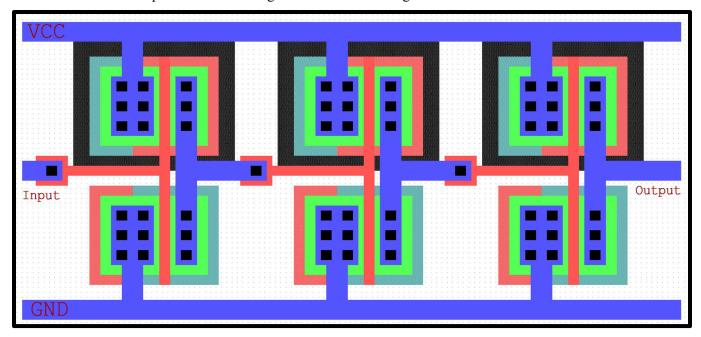


Figure-12: Cascaded CMOS Inverters

Here are the resulting cross section views for the cascaded CMOS Inverters as shown above.

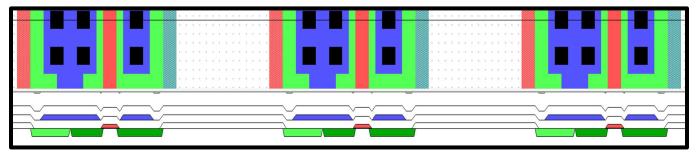


Figure-13: Horizontal Cross-Section of CMOS Inverter

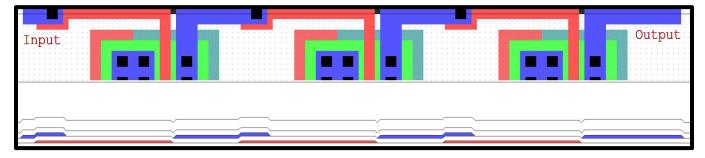


Figure-14: Horizontal Cross-Section of CMOS Inverter

DRC Files

The DRC files for the simulations are as follows:

###Procedures

```
MNMOS_DRC.txt-Notepad
File Edit Format View Help
DRC Errors in cell Cell0 of file C:\Users\RoderickLRenwick\Documents\03_mySchoolStuff\05_UMD_Fall_2019\ECE_413_VLSI\NMOS_Trial1.

0 errors.
DRC Merge/Gen Layers Elapsed Time: 0.000000 seconds.
DRC Test Elapsed Time: 0.000000 seconds.

DRC Elapsed Time: 0 seconds.
```

Figure-15: NMOS DRC File (total errors = 0)

```
PMOS_DRC.txt-Notepad
File Edit Format View Help
DRC Errors in cell Cell0 of file C:\Users\RoderickLRenwick\Documents\03_mySchoolStuff\05_UMD_Fall_2019\ECE_413_VLSI\assignments\finished\PMOS_TDB.

0 errors.
DRC Merge/Gen Layers Elapsed Time: 0.000000 seconds.
DRC Test Elapsed Time: 0.000000 seconds.
DRC Elapsed Time: 0 seconds.
```

Figure-16: PMOS DRC File (total errors = 0)

```
GMOS_INV_DRC.txt-Notepad
File Edit Format View Help
DRC Errors in cell Cell0 of file C:\Users\RoderickLRenwick\Documents\03_mySchoolStuff\05_UMD_Fall_2019\ECE_413_VLSI\CMOS_Trial_0.

0 errors.
DRC Merge/Gen Layers Elapsed Time: 0.000000 seconds.
DRC Test Elapsed Time: 0.000000 seconds.
DRC Elapsed Time: 0 seconds.
```

Figure-17: CMOS Inverter DRC File (total errors = θ)

```
□ CASCADED_CMOS_INV_DRC.txt - Notepad

□ CASCADED_CMOS_INV_DRC.txt - Notepad

□ X

File Edit Format View Help

DRC Errors in cell Cell0 of file C:\Users\RoderickLRenwick\Documents\03_mySchoolStuff\05_UMD_Fall_2019\ECE_413_VLSI\assignments\finished\CASCADED_CMOS_INV_TDB.

0 errors.

DRC Merge/Gen Layers Elapsed Time: 0.000000 seconds.

DRC Test Elapsed Time: 0.000000 seconds.

DRC Elapsed Time: 0 seconds.
```

Figure-18: Cascaded CMOS Inverters DRC File (total errors = 0)

Conclusion

Overall I think that this simulation is a fantastic way to learn about transistors and makes the topic very fun to learn about. I am enjoying the hands-on approach to constructing and design these transistors and I believe that it helps solidify the concepts immensely.