

# ECE 413: Intro to VLSI

## Assignment 5: Two-Bit Full Adder Design

Roderick Renwick



November 20, 2019  
Fall 2019

Honor Code:

I have neither given nor received unauthorized assistance on this graded report.

X \_\_\_\_\_ Roderick Renwick \_\_\_\_\_

# Table of Contents


<b>Table of Contents</b>	<b>2</b>
<b>Introduction</b>	<b>3</b>
<b>Design: One-Bit-Full-Adder</b>	<b>4</b>
<b>Design: NAND Gate</b>	<b>6</b>
<b>Design: XOR Gate</b>	<b>7</b>
<b>Design: INV Gate</b>	<b>8</b>
<b>Design: Two-Bit-Full-Adder</b>	<b>9</b>
<b>Implementation &amp; Simulation</b>	<b>10</b>
<b>L-Edit Results</b>	<b>15</b>
<b>DRC Verification</b>	<b>17</b>
<b>Conclusion</b>	<b>18</b>

## Introduction

The following laboratory procedure lays out the construction of a two-bit full adder and its transistor layout composed of CMOS inverters that are grouped into NAND and XOR logic gates.
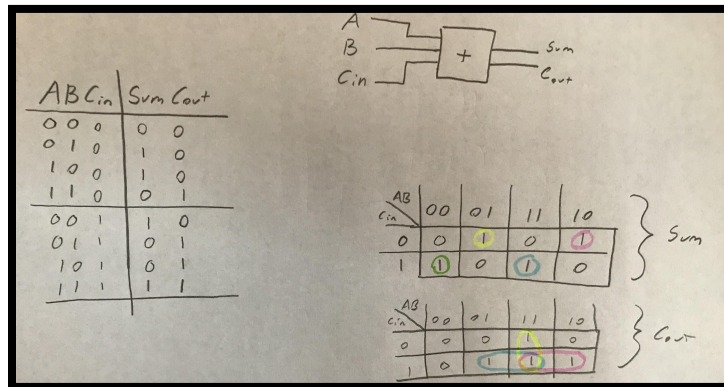
## Design: One-Bit-Full-Adder


To realize a two-bit-full-adder, the one-bit-full-adder must be designed first. The following figures provide the truth table, optimized kmap functions, and logic-gate layout for a one-bit-full-adder:




**One-Bit-Full-Adder Truth Table & K-Maps**

$$\begin{aligned}
 S_{um} &= \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C \\
 &= C(\overline{A}B + AB) + C'(\overline{A}B + AB) \\
 &= C(\overline{A}B + AB) + C'(A \oplus B) \\
 &= C(\overline{A \oplus B}) + C'(A \oplus B) \\
 &= A \oplus B \oplus C \\
 \\ 
 C_{out} &= AB + AC + BC \\
 &= AB + C(A + B) \\
 &= \overline{A}B + C(A \oplus B) \\
 &= (\overline{A}B)(C(A \oplus B))
 \end{aligned}$$

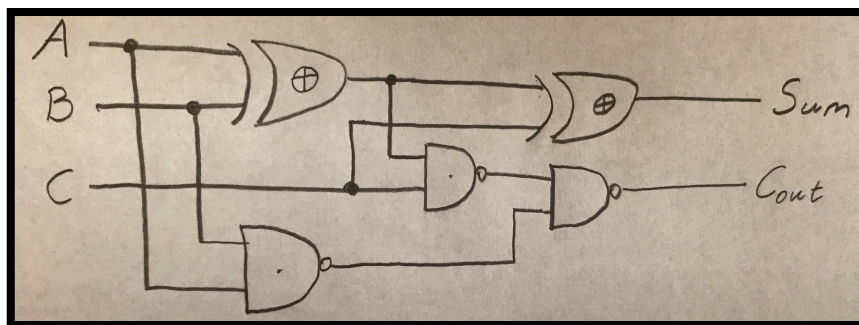**One-Bit-Full-Adder Boolean Algebra Optimization**



**One-Bit-Full-Adder Logic-Gate Design**

 



*Candidate Layout for One-Bit Adder Design*

## Design: NAND Gate

The truth table, optimized functions, circuit design, and transistor-level layout for a two-input NAND gate are as follows:

AB	$\overline{AB}$
00	1
01	1
10	1
11	0

$$\overline{AB} = (AB)'$$

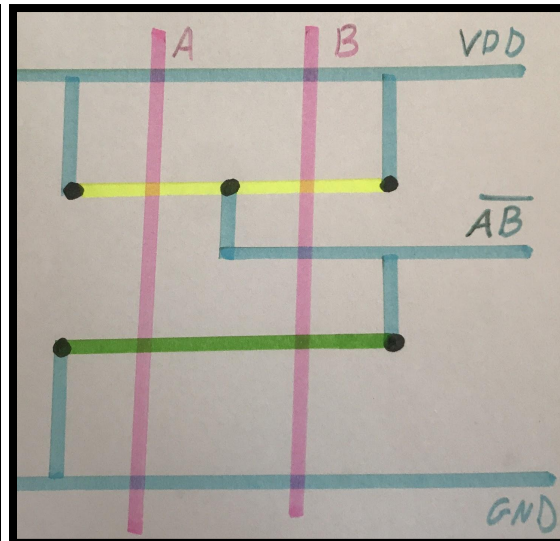
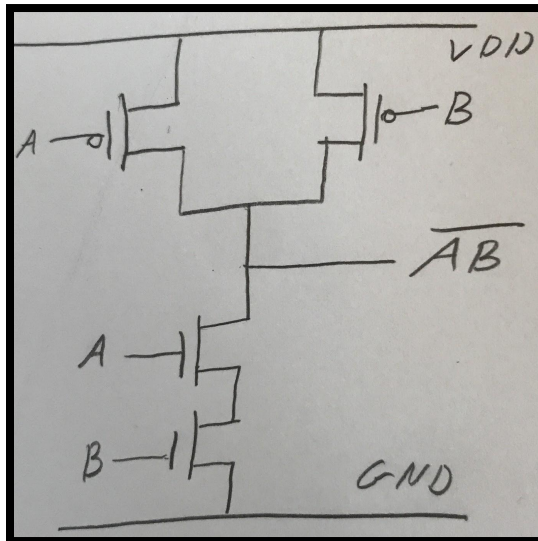


## Design: XOR Gate

The truth table, optimized functions, circuit design, and transistor-level layout for a two-input XOR gate are as follows:


AB	$A \oplus B$
00	0
01	1
10	1
11	0
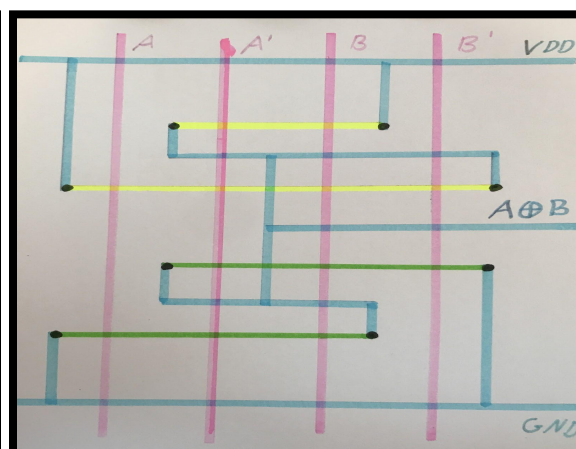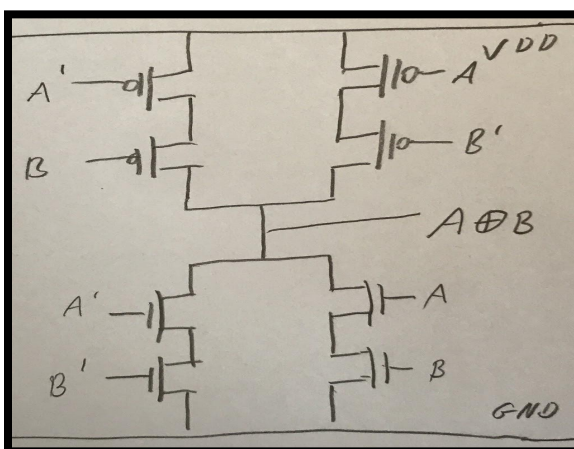
$$\begin{aligned}
 A \oplus B &= AB' + A'B \\
 &= ((\overline{AB'}) (\overline{A'B}))' \\
 &= ((A'+B)(A+B'))' \\
 &= (A'B' + AB)'
 \end{aligned}$$


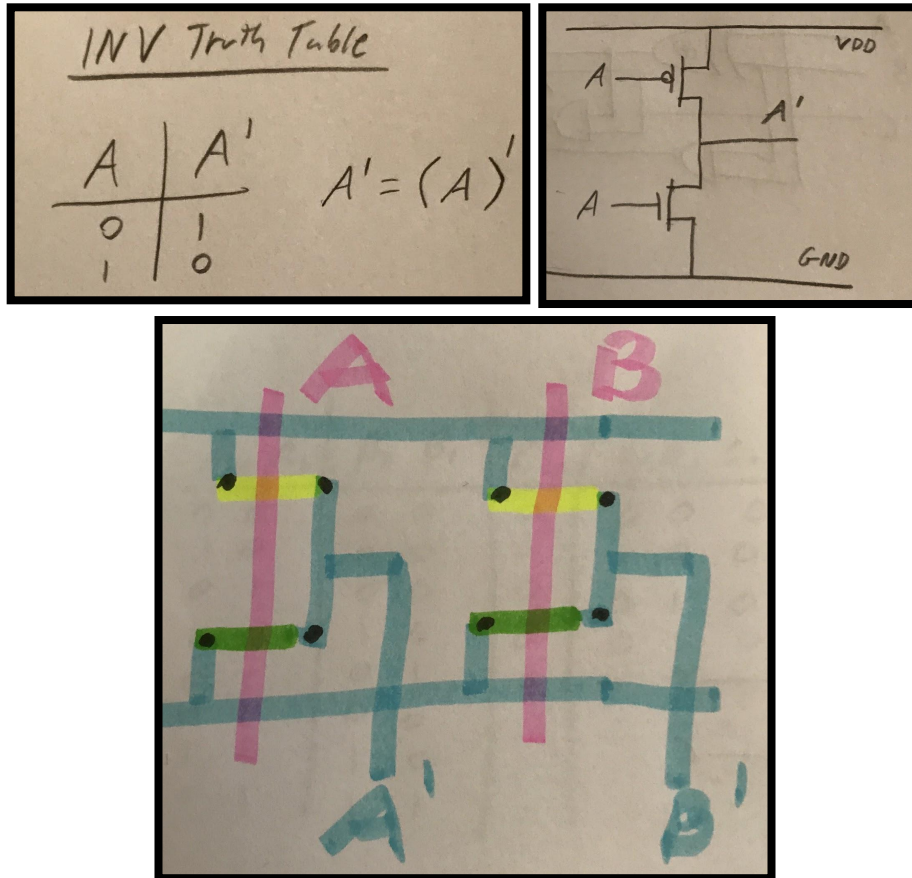
## Design: INV Gate

The truth table, optimized functions, circuit design, and transistor-level layout for an Inverter gate is as follows (note that this is done for both inputs A, and B):







## Implementation & Simulation

The following figures show the logical simulation of the two-bit-full-adder through valvalo software to verify and validate the design implementation:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

library UNISIM;
use UNISIM.VComponents.all;

entity nand2 is                                -- NAND_GATE ENTITY DECLARATION
    port (
        i0, i1 : in std_logic;
        o : out std_logic
    );
end nand2;

architecture behaviour of nand2 is           -- NAND_GATE ARCHITECTURE DECLARATION
begin
    o <= not ( i0 and i1 );                  -- NAND_GATE BEHAVIORAL STATEMENT
end behaviour;

-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

library UNISIM;
use UNISIM.VComponents.all;

entity xor2 is                                -- XOR_GATE ENTITY DECLARATION
    port (
        i0, i1 : in std_logic;
        o : out std_logic
    );
end xor2;

architecture behaviour of xor2 is           -- XOR_GATE ARCHITECTURE DECLARATION
begin
    o <= not ( ( not ( ( not ( i0 and i1 ) ) and i0 ) ) and ( not ( not ( i0 and i1 ) ) and i1 ) );
end behaviour;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

library UNISIM;
use UNISIM.VComponents.all;

entity one_bit_addr is -- 2-bit adder ENTITY DECLARATION
  Port (
    X_in : in STD_LOGIC;
    Y_in : in STD_LOGIC;
    C_in : in STD_LOGIC;
    S_out : out STD_LOGIC;
    C_out : out STD_LOGIC
  );
end one_bit_addr;

architecture struct of one_bit_addr is-- 2-bit adder ARCHITECTURE DECLARATION

  component nand2 -- NAND_GATE Component Declaration
  port (
    i0, i1: in std_logic;
    o : out std_logic
  );
end component;
  component xor2 -- XOR_GATE component declaration
  port (
    i0, i1 : in std_logic;
    o : out std_logic
  );
end component;

```

```

-- Internal Signals Declarations
signal xor0 : std_logic;
signal nand0 : std_logic;
signal nand1 : std_logic;

begin

  -- Component Instantiations Statements
  u0 : nand2 port map ( i0 => X_in, i1 => Y_in, o => nand0 );
  u1 : nand2 port map ( i0 => xor0, i1 => C_in, o => nand1 );
  u2 : nand2 port map ( i0 => nand0, i1 =>nand1, o => C_out );
  u3 : xor2 port map ( i0 => X_in, i1 => Y_in, o => xor0 );
  u4 : xor2 port map ( i0 => xor0, i1 => C_in, o => S_out );

end struct;

```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

library UNISIM;
use UNISIM.VComponents.all;

entity two_bit_addr is -- 2-bit adder ENTITY DECLARATION
  Port (
    X0_in : in STD_LOGIC;
    Y0_in : in STD_LOGIC;
    X1_in : in STD_LOGIC;
    Y1_in : in STD_LOGIC;
    C_in  : in STD_LOGIC;
    C_out : out STD_LOGIC;
    S0_out : out STD_LOGIC;
    S1_out : out STD_LOGIC
  );
end two_bit_addr;

architecture struct of two_bit_addr is-- 2-bit adder ARCHITECTURE DECLARATION

  component one_bit_addr -- NAND_GATE Component Declaration
  port (
    X_in, Y_in, C_in: in std_logic;
    C_out, S_out : out std_logic
  );
  end component;

  -- Internal Signals Declarations
  signal c_out_signal : std_logic;

begin

  -- Component Instantiations Statements
  u0 : one_bit_addr port map ( X_in => X0_in, Y_in => Y0_in, C_in => C_in, C_out => c_out_signal, S_out => S0_out );
  u1 : one_bit_addr port map ( X_in => X1_in, Y_in => Y1_in, C_in => c_out_signal, C_out => C_out, S_out => S1_out );

end struct;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

library UNISIM;
use UNISIM.VComponents.all;

entity two_bit_addr_tb is
end two_bit_addr_tb;

architecture two_bit_addr_tb of two_bit_addr_tb is

    component two_bit_addr is
        Port (
            X0_in  : in  STD_LOGIC;
            Y0_in  : in  STD_LOGIC;
            X1_in  : in  STD_LOGIC;
            Y1_in  : in  STD_LOGIC;
            C_in   : in  STD_LOGIC;
            C_out  : out STD_LOGIC;
            S0_out : out STD_LOGIC;
            S1_out : out STD_LOGIC
        );
    end component;

    signal X0_in  : std_logic := '0';
    signal X1_in  : std_logic := '0';
    signal Y0_in  : std_logic := '0';
    signal Y1_in  : std_logic := '0';
    signal C_in   : std_logic := '0';
    signal C_out  : std_logic;
    signal S0_out : std_logic;
    signal S1_out : std_logic;

```

```



begin

    UUT : two_bit_addr
    port map (
        X0_in => X0_in, X1_in => X1_in, Y0_in => Y0_in, Y1_in => Y1_in, C_in => C_in,
        C_out => C_out, S0_out => S0_out, S1_out => S1_out
    );

    X0_in <= NOT X0_in after 5 ns;
    X1_in <= NOT X1_in after 10 ns;
    Y0_in <= NOT Y0_in after 20 ns;
    Y1_in <= NOT Y1_in after 40 ns;


end two_bit_addr_tb;

```

 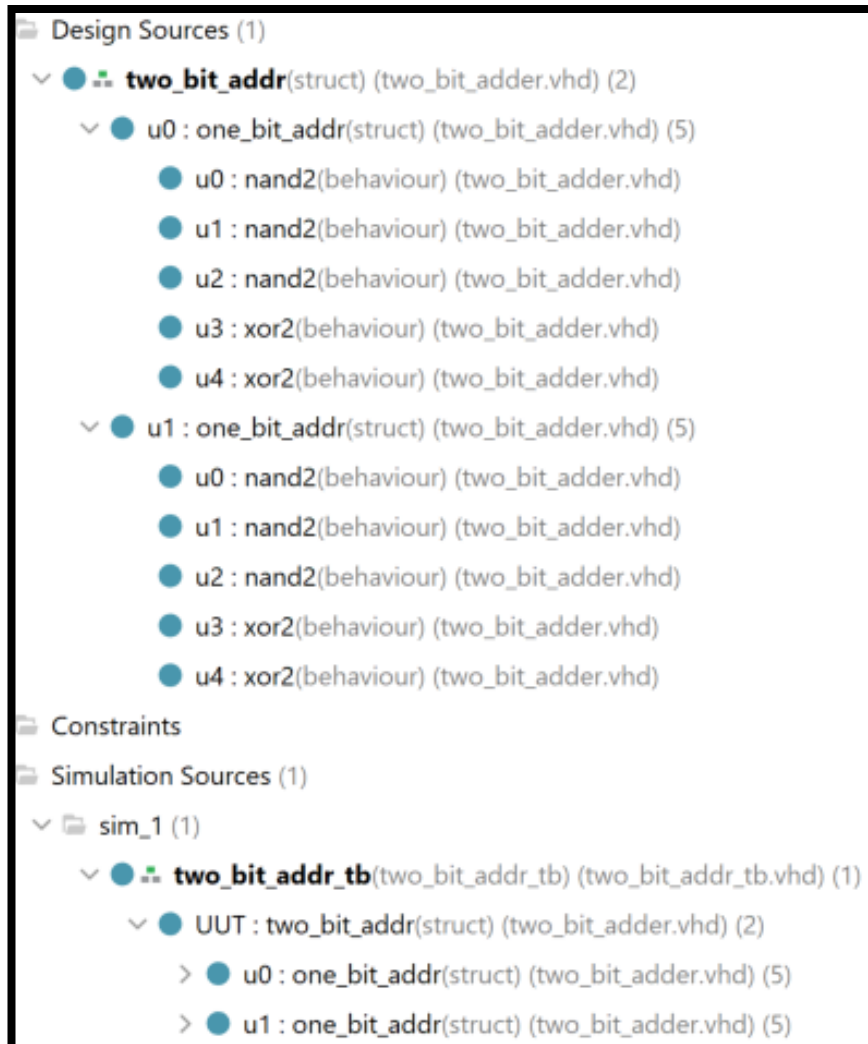

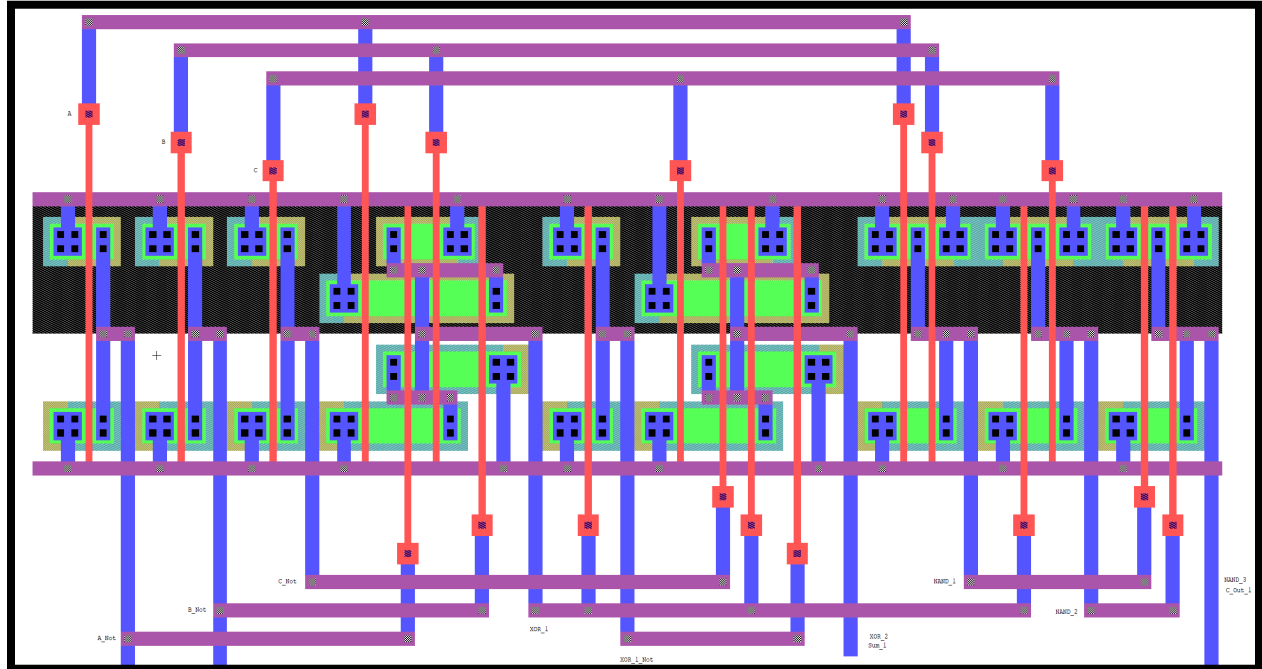
## L-Edit Results

Here is the resulting L-Edit layout of a one-bit-full-adder:



 
Here is the resulting L-Edit layout of a two-bit-full-adder, after connecting two one-bit-full-adders together as laid out in the design steps above:





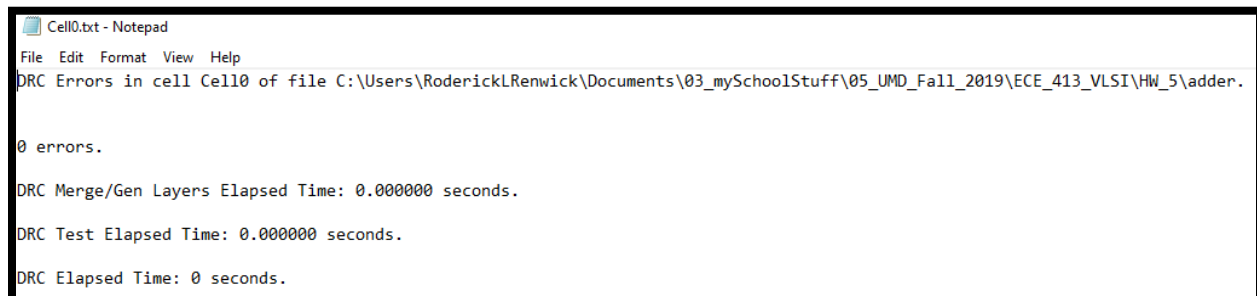
## DRC Verification

Here are the resulting DRC check verification messages and file:



The screenshot shows a Notepad window titled "Cell0.txt - Notepad". The menu bar includes "File", "Edit", "Format", "View", and "Help". The text content of the file is as follows:
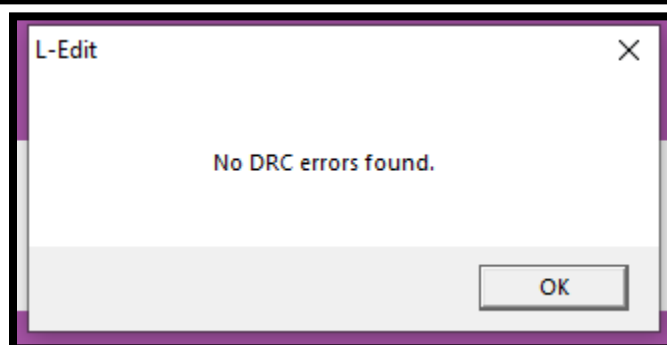
```
DRC Errors in cell Cell0 of file C:\Users\RoderickLRenwick\Documents\03_mySchoolStuff\05_UMD_Fall_2019\ECE_413_VLSI\HW_5\adder.  
  
0 errors.  
  
DRC Merge/Gen Layers Elapsed Time: 0.000000 seconds.  
  
DRC Test Elapsed Time: 0.000000 seconds.  
  
DRC Elapsed Time: 0 seconds.
```



## Conclusion

The homework was successfully verified and validated from both the software implementation in Valvado, and the hardware layout design in L-Edit. Overall, I learned a lot from this lab. It really challenged me to think carefully and plan ahead for the layout from start to finish.